

Electricity Knowledge Organiser – Year 4 – Autumn 2 – Science

I understand the dangers of electricity

- Plugging in too many things in a socket
- Bare wires (with no plastic coating)
- Fingers in sockets
- Wires dangling or trailing on carpet
- Water near electrical appliances or wires (water conducts electricity)



I understand conductors and insulators

Electrical Conductors (allow electricity to flow)

Electrical Insulators (don't allow electricity to flow)




Copper
Iron
Steel
Silver
Gold

Rubber
Wood
Plastic
Paper

I can identify some common appliances that run on electricity



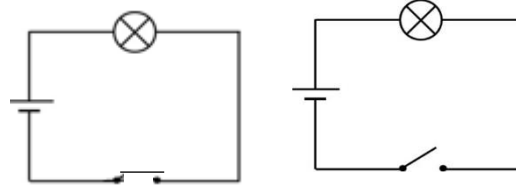I can explain how a switch works
I can draw a simple circuit diagram using symbols and explain if it will work or not




The light bulb will light in this circuit because the switch is closed.


The light bulb will not light in this circuit because the switch is open.



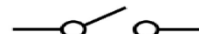Closed switch - electricity will flow because the circuit is complete



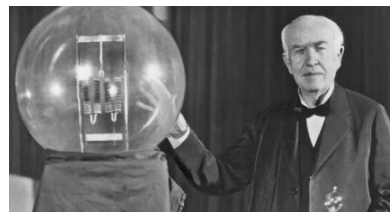Open switch - electricity won't flow because the circuit is not complete.



Thomas Edison is an American scientist and inventor. He invented his most famous invention in 1879.

Vocabulary I can name and can use electrical circuit symbols

Lamp

A lamp will light up when the circuit is connected correctly.




Wire

A long thin piece of metal that carries an electrical current often covered in plastic for safety.




Cell

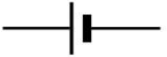A battery is an example of a cell. It provides electricity



Battery

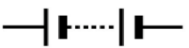A small device that provides power for electrical items.



Motor

A device that changes electrical energy into



Buzzer

An electrical device that makes a buzzing sound.



Switch

A switch allows an electrical device to be turned on and off

Current

A flow of electricity through a wire.

Circuit

A circuit is a complete path around which electricity can flow. It must include a source of electricity, such as a battery.